

E8-262 Lecture 11

D. Gope

Ref: ① C. Paul  
Chap 8  
② Hall and Heek  
Chap 3

$$\frac{\partial V(z,t)}{\partial z} = -l \frac{\partial I(z,t)}{\partial t}$$

$$\frac{\partial I(z,t)}{\partial z} = -c \frac{\partial V(z,t)}{\partial t}$$

$$\frac{\partial^2 V(z,t)}{\partial z^2} = lc \frac{\partial^2 V(z,t)}{\partial t^2}$$

$$\frac{\partial^2 I(z,t)}{\partial z^2} = lc \frac{\partial^2 I(z,t)}{\partial t^2}$$

$$V(z,t) = V^+(t - \frac{z}{v}) + V^-(t + \frac{z}{v})$$


$$I(z,t) = I^+(t - \frac{z}{v}) + I^-(t + \frac{z}{v})$$

$$= \frac{V^+}{Z_0} (t - \frac{z}{v}) - \frac{V^-}{Z_0} (t + \frac{z}{v})$$

$$v = \frac{1}{\sqrt{lc}}$$

$$Z_0 = \sqrt{\frac{l}{c}}$$

# Time domain analysis: Wave tracing

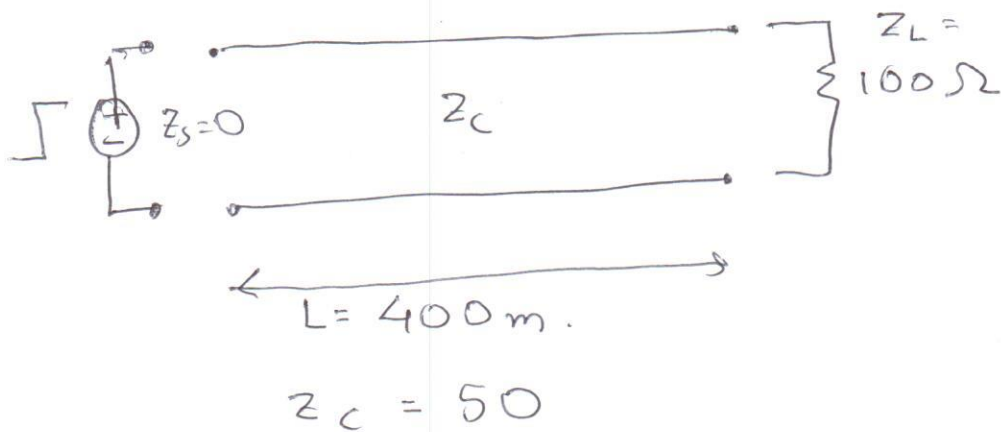


$$\Gamma_L = \frac{100 - 50}{100 + 50} = \frac{1}{3}$$


$$\Gamma_S = \frac{0 - 50}{0 + 50} = -1$$

$$T_D = \frac{L}{v} = \frac{400 \text{ m}}{200 \times 10^6 \text{ m/s}} = 2 \mu\text{s}$$

At  $t = 1 \mu\text{s}$

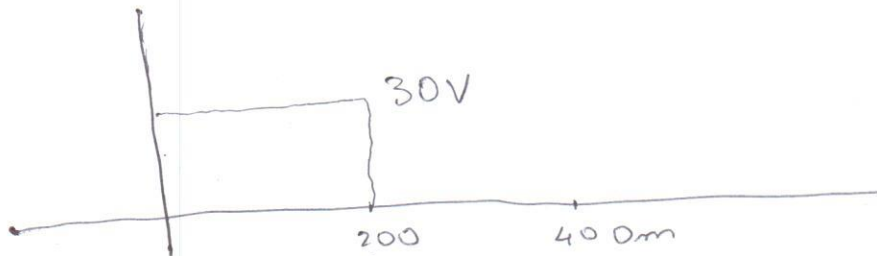

At  $t = 2.5 \mu\text{s}$

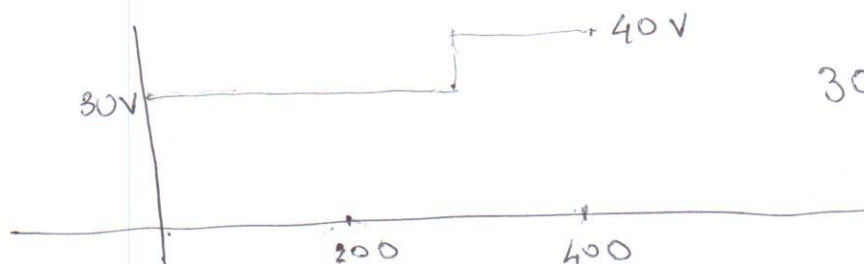


$$30 \Gamma_L = 10$$

At  $t = 4.5 \mu\text{s}$



$$\Gamma_S 10 = -10$$

# Lattice diagrams

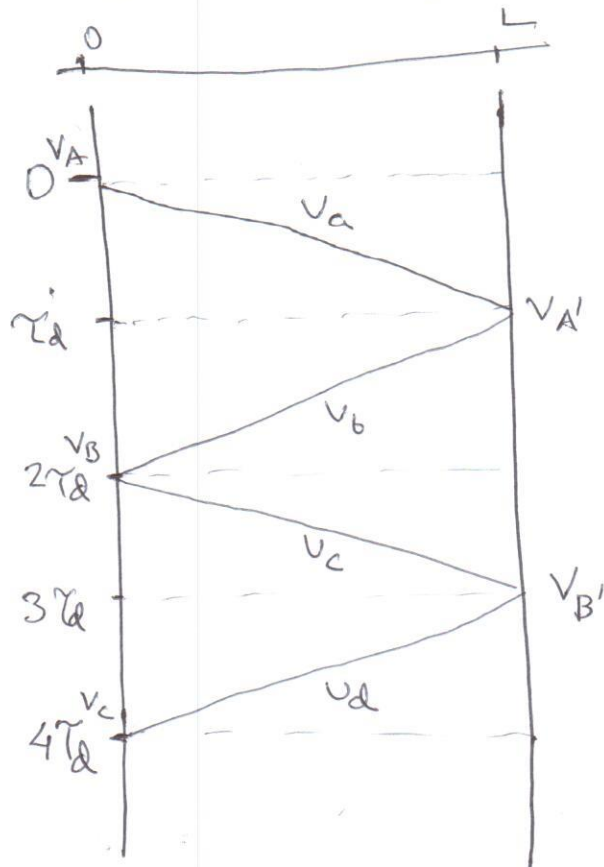



$$V_A = V_a \quad V_B = V_a + V_b + V_c \quad V_C = V_a + V_b + V_c + V_d + V_e$$

$$V_a = V_s \frac{Z_0}{Z_0 + R_s}$$



$$V_b = V_a \Gamma_L$$

$$V_c = V_b \Gamma_0$$

# Underdriven and overdriven line

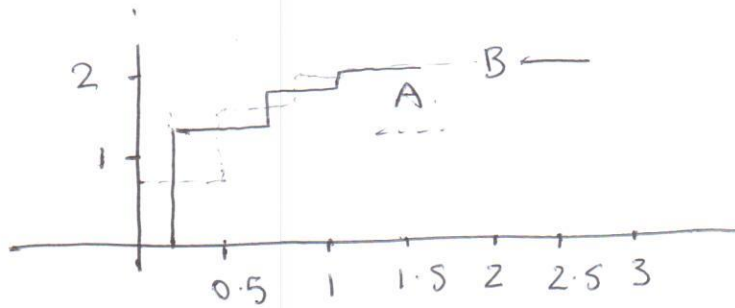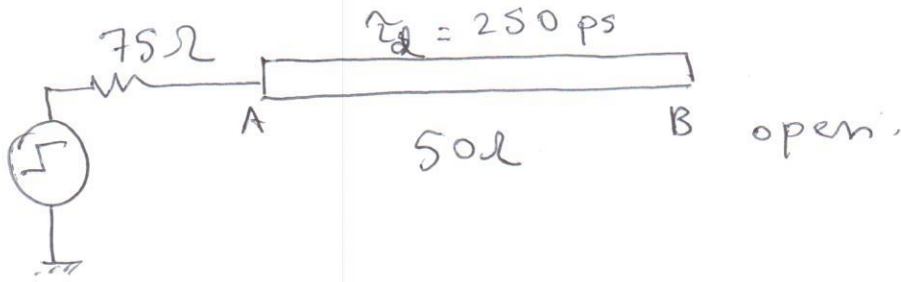

underdriven

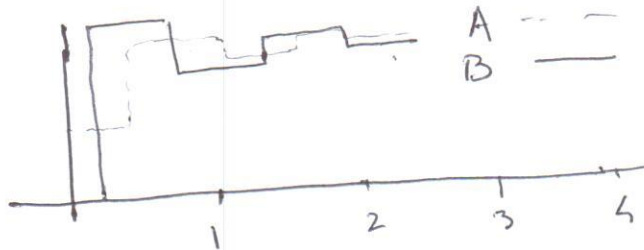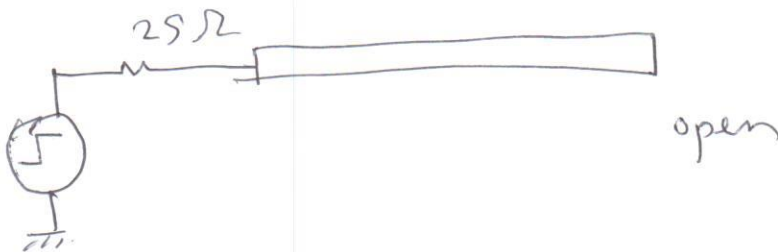

overdriven

$V_S$

-

+

-

+


$P_{T_L}$

+

-

-

+

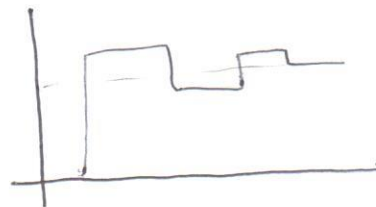


overdriven



underdriven

# Cascaded Tx lines

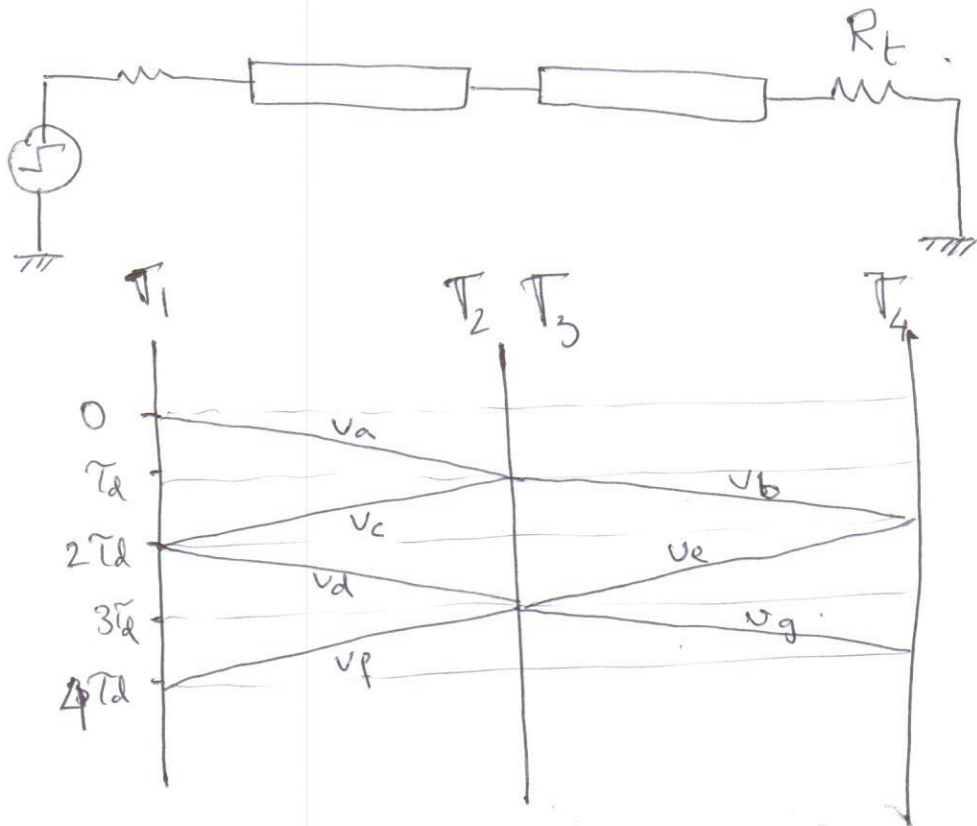


$$v_a = v_s \frac{Z_{01}}{Z_{01} + R_s}$$

$$v_b = v_a T_2$$

$$v_c = v_a T_2$$

What is  $T$ ?

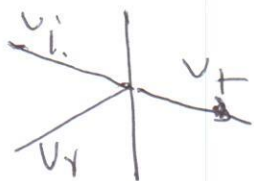

$$v_i = v_i^+ e^{-j\beta_1 z}$$


$$v_r = v_r^- e^{+j\beta_1 z}$$

$$j\beta_2 z$$


$$v_r = T v_i$$

$$v_t = v_i + v_r$$

# Time domain reflectometry (TDR)

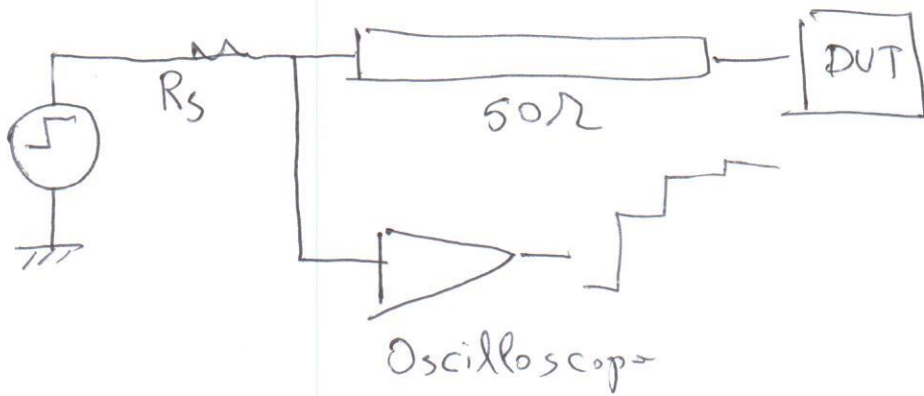

Output —  $Z_0$  and  $\Gamma$ .

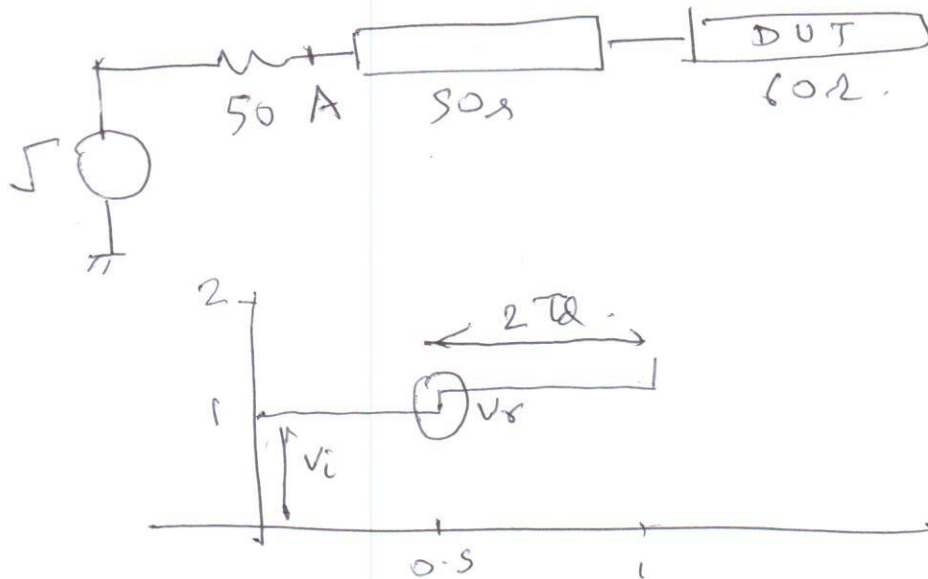

$$\Gamma = \frac{V_r}{V_i} = \frac{Z_{DUT} - Z_0}{Z_{DUT} + Z_0}$$

$$Z_{DUT} = Z_0 \frac{V_i + V_r}{V_i - V_r}$$

$$Z_{DUT} = 50 \frac{1 + 0.091}{1 - 0.091} = 60\Omega$$

# SPICE simulation

Method of characteristics  
or Branin's method



$$\begin{cases} V(z, t) = V^+ \left( t - \frac{z}{v} \right) + V^- \left( t + \frac{z}{v} \right) \\ z_c I(z, t) = V^+ \left( t - \frac{z}{v} \right) - V^- \left( t + \frac{z}{v} \right) \end{cases}$$

$$\begin{cases} V(z, t) + z_c I(z, t) = 2V^+ \left( t - \frac{z}{v} \right) \\ V(z, t) - z_c I(z, t) = 2V^- \left( t + \frac{z}{v} \right) \end{cases}$$

$$\begin{cases} V(0, t) + z_c I(0, t) = 2V^+(t) \\ V(0, t) - z_c I(0, t) = 2V^-(t) \\ V(L, t) + z_c I(L, t) = 2V^+(t - T_D) = 2D^+ V^+(t) \\ V(L, t) - z_c I(L, t) = 2V^-(t + T_D) = 2D^- V^-(t) \end{cases}$$

$$V(0,t) - Z_c I(0,t) = V(L,t - T_D) - Z_c I(L,t - T_D)$$
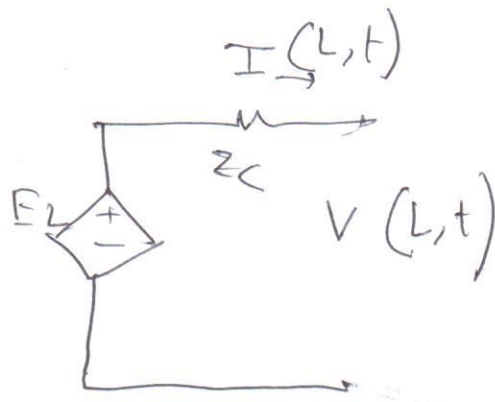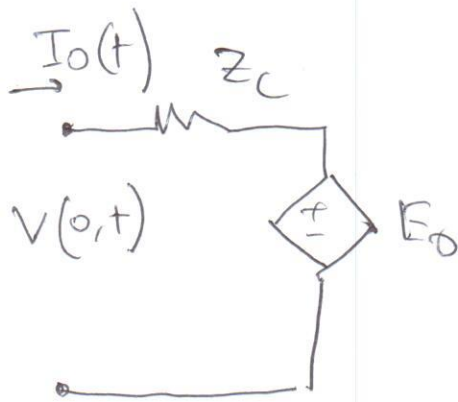
$$V(L,t) + Z_c I(L,t) = V(0,t - T_D) + Z_c I(0,t - T_D)$$



$$E_0 = V(L,t - T_D) - Z_c I(L,t - T_D)$$

$$E_L = V(0,t - T_D) + Z_c I(0,t - T_D)$$

Stamps ?



Freq dependant :- lossy Tx line.

$$\frac{dV(z, \omega)}{dz} = - \left[ r(\omega) - j\omega l_i(\omega) \right] I(z, \omega) - j\omega l I(z, \omega)$$

$$\frac{dV(z, t)}{dz} = - z_i * I(z, t) - l \frac{\partial I(z, t)}{\partial t}$$

$$z_i * I(z, t) = \int_0^t z_i(\tau) I(z, t-\tau) d\tau$$

① How to get  $z(\tau)$

② ~~convolution~~ convolution.