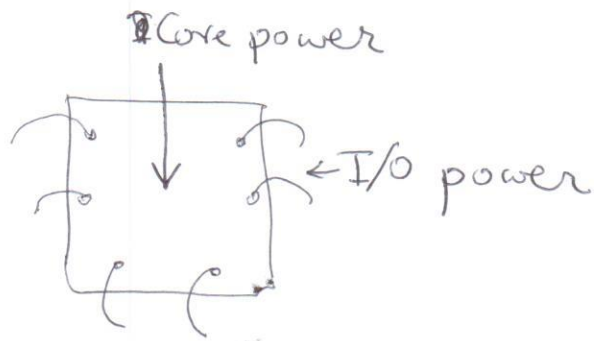


E8: 262 Lecture 16

Power Integrity: AC analysis

Core power vs. I/O power



Core power - power supply to core circuits

I/O power - power supply to I/O circuits

Target Impedance:-

$$Z_T = \frac{V_{dd} \times \text{ripple}}{50\% \text{ of } I_{max}}$$

e.g. ripple = 5% of 5V. V_{dd}

$$I_{max} = 1$$

$$Z = 0.5 \Omega$$


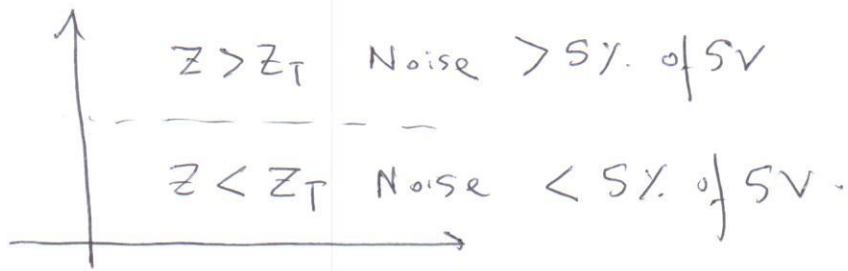


Table 1.1 of Ref.


	V	Power	Current	Z target	F (MHz)
1990	5	5	1	250	16
2002	1.2	180	150	0.4	1200

Components of a PDN

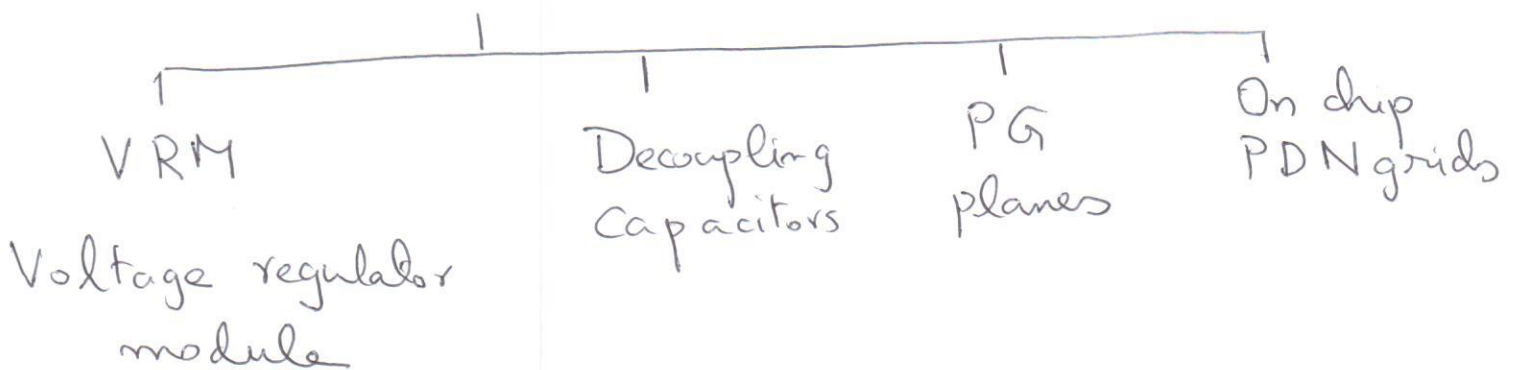

Modeling Power ground planes

(a) Transmission line models

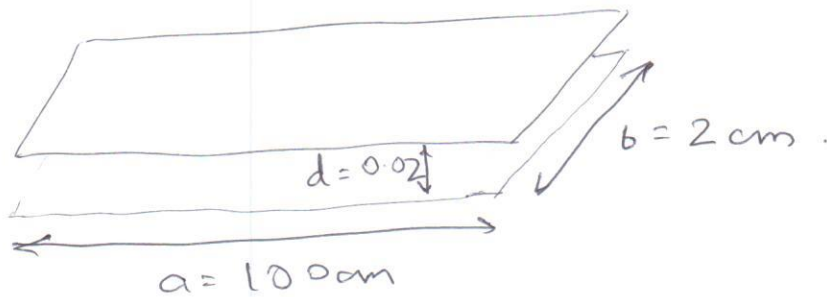

$$C = \frac{\epsilon_0 b}{d} = 8.854 \text{ pF/cm}$$

$$L = \frac{\mu_0 d}{b} = 0.125 \text{ nH/cm}$$

$$Z_0 = \sqrt{\frac{L}{C}} = 3.757 \Omega$$

$$T_d = a \sqrt{LC} = 3.33 \text{ ns/cm}$$

$$Z_{in} = Z_0 \left[\frac{Z_L + j Z_0 \tan \beta a}{Z_0 + j Z_L \tan \beta a} \right]$$

$$Z_L = \infty$$

For $a = \frac{\lambda}{4}$ resonance $Z_{in} = 0$

$a = \frac{\lambda}{2}$ anti-resonance $Z_{in} = \infty$


(b) Multilayered Finite Difference Method

(MFDM) - Ref:- Engin et al. IEEE Trans
on EMC pp. 441 - 448

$$\text{eq}^n: (\nabla_T^2 + k^2)u = -j\omega \mu d J_z$$

Unit cell model for a plane pair:-

Unit cell model:

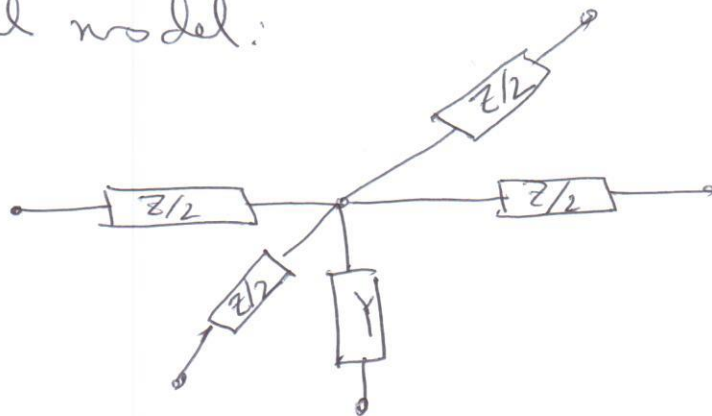

$$Z = R + j\omega L$$

$$Y = G + j\omega C$$

$$C = \frac{\epsilon h^2}{d}$$

$$L = \mu d$$



h = cell size

d = plane distance.


$$R = \frac{2}{\sigma t} + 2 \sqrt{\frac{j\omega \mu}{\sigma}}$$

$$G = \omega C \tan \delta$$

Multi planar structures

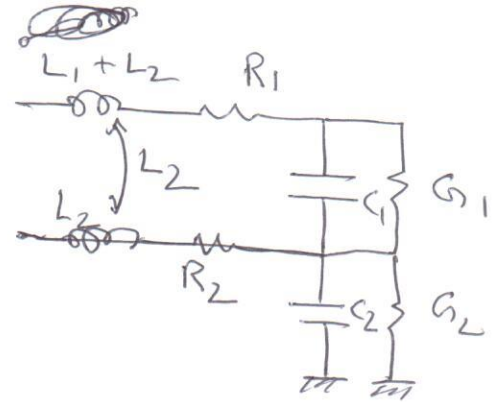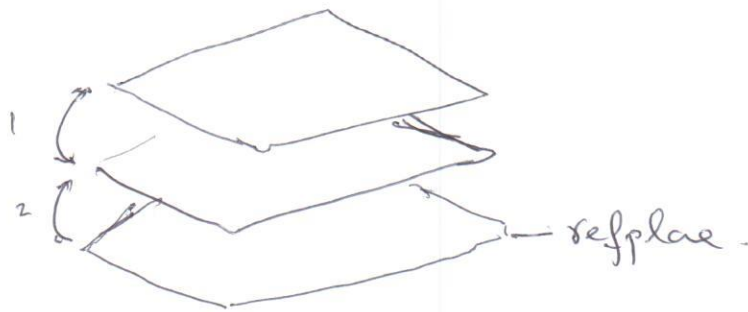

Implementation:

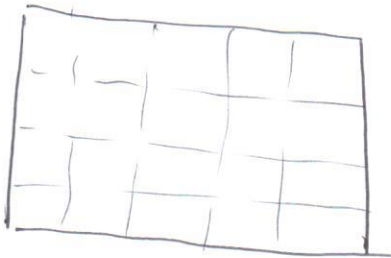

(a) discretization.

(b) identify ref. plane.

(c) stamp R, L, C, G.

(d) solve as MNA.

Drawbacks :-

- (a) Horizontal coupling: fringe and gap.
- (b) Ref plane identification.

Extension to non-uniform meshing

Mosim et al. ISQED 2010.

"Efficient Hierarchical discretization of
off-chip power delivery Network geom.
for 2.5D Electrical analysis.