

Two conductor Tx line

Freq domain analysis.

Eqn:

$$\frac{dV(z)}{dz} = -(r + j\omega l) I(z)$$

$$\frac{dI(z)}{dz} = -(g + j\omega c) V(z)$$

Lossless ∴ both  $r = 0$  &  $g = 0$ .

$\beta, v, Z_c$

$$\frac{dV(z)}{dz} = -j\omega l I(z); \quad \frac{dI(z)}{dz} = -j\omega c V(z).$$

$$\frac{d^2V}{dz^2} = -\omega^2 l c V \Rightarrow V(z) = V^+ e^{-j\beta z} + V^- e^{j\beta z}$$

phase const.  $\beta = \omega \sqrt{lc}$

phase vel  $v = \frac{1}{\sqrt{lc}}$

$$I(z) = I^+ e^{-j\beta z} + I^- e^{j\beta z}$$

$$I^+ = \frac{V^+}{Z_c} \quad I^- = -\frac{V^-}{Z_c}$$

$$Z_c = \sqrt{\frac{L}{C}} \quad \text{how?}$$



characteristic impedance.

$\Gamma$  and  $Z_{in}$ .

$$\Gamma(z) = \frac{V^- e^{j\beta z}}{V^+ e^{-j\beta z}} = \frac{V^-}{V^+} e^{j2\beta z}.$$

$$V(z) = V^+ e^{-j\beta z} [1 + \Gamma(z)]$$

$$I(z) = \frac{V^+}{Z_c} e^{-j\beta z} [1 - \Gamma(z)]$$

At  $z = L$   $\Gamma_L = \frac{V^-}{V^+} e^{j2\beta L}$

$$Z_L = Z_c \left[ \frac{1 + \Gamma(L)}{1 - \Gamma(L)} \right]$$

$$\Gamma_L = \frac{Z_L - Z_c}{Z_L + Z_c}$$

$$\Gamma(z) = \Gamma(L) e^{j2\beta(z-L)}$$

$$\Rightarrow V(z) = V^+ e^{-j\beta z} \left[ 1 + \Gamma_L e^{j2\beta(z-L)} \right]$$

$$I(z) = \frac{V^+}{Z_c} e^{-j\beta z} \left[ 1 - \Gamma_L e^{j2\beta(z-L)} \right]$$

$$Z_{in} = \frac{V(z)}{I(z)} = Z_c \frac{[1 + \Gamma(z)]}{[1 - \Gamma(z)]}$$

$$Z_{in}(0) = Z_c \frac{[1 + \Gamma(0)]}{[1 - \Gamma(0)]}$$

$$= Z_c \left[ \frac{1 + \Gamma_L e^{-j2\beta L}}{1 - \Gamma_L e^{-j2\beta L}} \right]$$

Use  $\Gamma_L e^{-2j2\beta L} = \frac{\Gamma_L e^{-j\beta L}}{e^{+j\beta L}} = \frac{(Z_L - Z_c) e^{-j\beta L}}{(Z_L + Z_c) e^{+j\beta L}}$

$$Z_{in}(0) = Z_c \frac{Z_L + jZ_c \tan(\beta L)}{Z_c + jZ_L \tan(\beta L)}$$

$$L = \frac{\pi}{4}$$


$$Z_{in}(0) = \frac{Z_0^2}{Z_L}$$

$$L = n \frac{\pi}{2}$$

$$Z_{in}(0) = Z_L$$

$$Z_{in}\left(z \pm n \frac{\pi}{2}\right) = Z_{in}(z)$$

# ABCD, Z, Y parameters

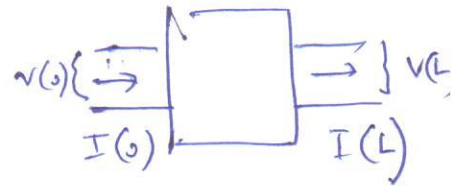

$$\begin{bmatrix} V(L) \\ I(L) \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V(0) \\ I(0) \end{bmatrix}$$

$$\begin{bmatrix} V(0) \\ I(0) \end{bmatrix} = \begin{bmatrix} 1 & 1 \\ \frac{1}{Z_c} & -\frac{1}{Z_c} \end{bmatrix} \begin{bmatrix} V^+ \\ V^- \end{bmatrix}$$


$$\begin{bmatrix} V(L) \\ I(L) \end{bmatrix} = \begin{bmatrix} e^{-j\beta L} & e^{j\beta L} \\ \frac{1}{Z_c} e^{-j\beta L} & -\frac{1}{Z_c} e^{j\beta L} \end{bmatrix} \begin{bmatrix} V^+ \\ V^- \end{bmatrix}$$

$$\Rightarrow \begin{bmatrix} V(L) \\ I(L) \end{bmatrix} = \begin{bmatrix} e^{-j\beta L} & e^{j\beta L} \\ \frac{1}{Z_c} e^{-j\beta L} & -\frac{1}{Z_c} e^{j\beta L} \end{bmatrix} \begin{bmatrix} 1 & 1 \\ \frac{1}{Z_c} & -\frac{1}{Z_c} \end{bmatrix}^{-1} \begin{bmatrix} V(0) \\ I(0) \end{bmatrix}$$

$$= \begin{bmatrix} e^{-j\beta L} & e^{j\beta L} \\ \frac{1}{Z_c} e^{-j\beta L} & -\frac{1}{Z_c} e^{j\beta L} \end{bmatrix} \frac{1}{Z_c} \begin{bmatrix} 1 & Z_c \\ 1 & -Z_c \end{bmatrix} \begin{bmatrix} V(0) \\ I(0) \end{bmatrix}$$

$$= \begin{bmatrix} \cos(\beta L) & -j Z_c \sin(\beta L) \\ -j \frac{\sin(\beta L)}{Z_c} & \cos(\beta L) \end{bmatrix} \begin{bmatrix} V(0) \\ I(0) \end{bmatrix}$$

Z parameters:

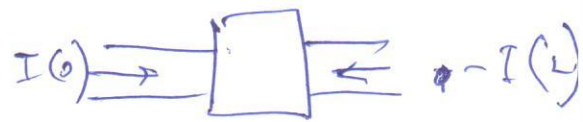

$$\begin{bmatrix} V(0) \\ V(L) \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I(0) \\ -I(L) \end{bmatrix}$$

$$V(L) = \cos(\beta L) V(0) - j Z_c \sin(\beta L) I(0)$$

$$I(L) = -j \frac{\sin \beta L}{Z_c} V(0) + \cos(\beta L) I(0)$$

$$\Rightarrow V(L) = \cos(\beta L) \left[ -\frac{Z_c I(L)}{j \sin \beta L} + \frac{Z_c \cos \beta L}{j \sin \beta L} I(0) \right] - j Z_c \sin \beta L I(0)$$

$$\Rightarrow V(L) = \frac{Z_c \cos(\beta L)}{j \sin(\beta L)} \left[ I(L) \right] + \frac{Z_c (\cos^2 \beta L + \sin^2 \beta L)}{j \sin \beta L} I(0)$$

$$Z = \begin{bmatrix} \frac{Z_c \cos(\beta L)}{j \sin(\beta L)} & \frac{Z_c}{j \sin(\beta L)} \\ \frac{Z_c}{j \sin(\beta L)} & \frac{Z_c \cos(\beta L)}{j \sin(\beta L)} \end{bmatrix}$$


~~SPICE~~ SPICE simulation, lossless

Tx    N1    N2    N3    N4     $Z = Z_C$      $T_D = T_D$

Stamp of spice matrix  $\equiv Z$  or  $Y$ .

$Z$  parameters depend on  $(\beta L)$  and  $Z_C$
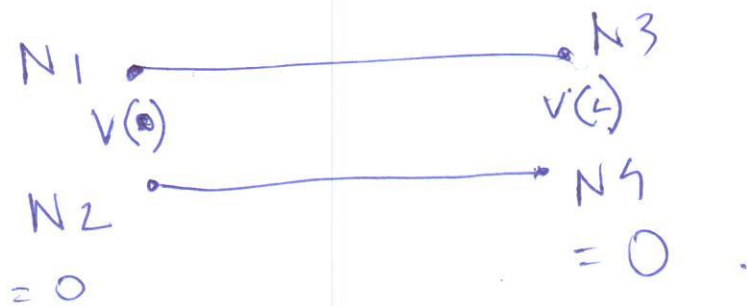
$$\beta L = \omega \sqrt{\epsilon_c} L = \frac{\omega}{v} L = \omega T_D.$$



$$\begin{pmatrix} I(0) \\ I(L) \end{pmatrix} = Y \begin{pmatrix} V_0 \\ V_L \end{pmatrix}$$

lossy line :-

$$\frac{dV(z)}{dz} = -z I(z)$$

$$\frac{dI(z)}{dz} = -y V(z)$$

$$\frac{d^2V(z)}{dz^2} = zy V(z); \quad \frac{d^2I(z)}{dz^2} = yz I(z)$$

$$\gamma = \sqrt{zy} = \sqrt{(r+j\omega L)(g+j\omega C)}$$
$$= \alpha + j\beta$$

$$V(z) = V^+ e^{-\gamma z} + V^- e^{+\gamma z}$$


$$Z_c = \sqrt{\frac{z}{y}} = \sqrt{\frac{r+j\omega L}{g+j\omega C}}$$



# SPICE lossy transmission line
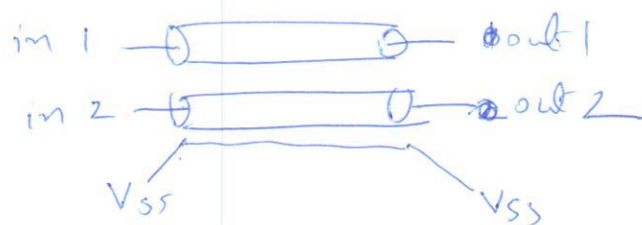
## W element modeling

Wline1 in1 in2 Vss out1 out2 Vss  
+ RLG Cmodel = 'modelname' N=2 L=0.1




Include GDimag = 75

.MODEL ~~W~~ model name Model Type = RLG C N=1  
+ L0 = 3.8e-7  
+ C0 = 1.3e-10  
+ R0 = 2.74e0  
+ G0 = 0  
+ RS = 1e-3  
+ GD = 0.07  
+ wp = 0.07

$$R(f) = R_0 + \sqrt{f} (1+j) R_s$$

$$G(\omega) = G_0 + \sum_k G_{dk} \frac{j\omega}{j\omega + \omega_{pk}}$$

Pi model

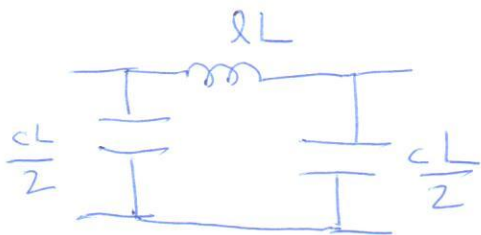

T model

